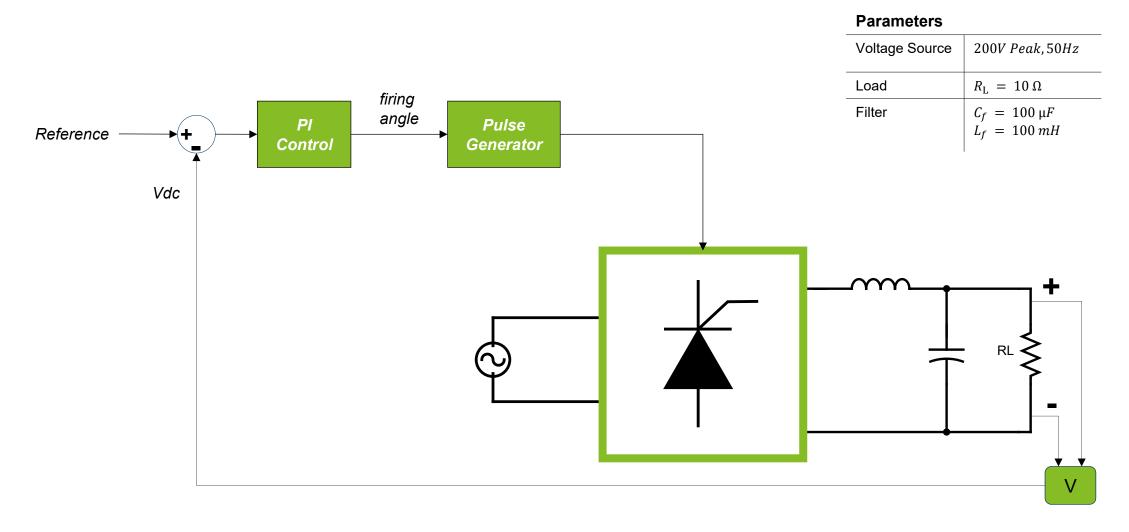


# DC Voltage Controller




## **Block diagram of DC Voltage Control**


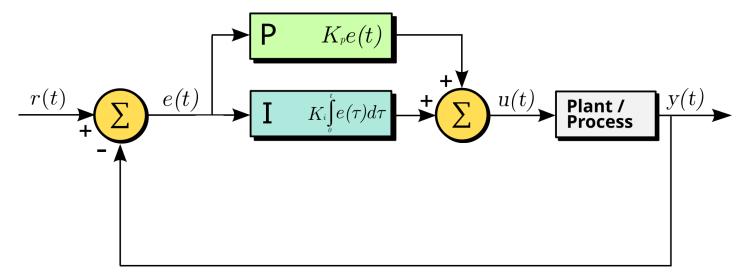
### **PI** Control

PI control is a feedback back based control loop.



- Proportional (P): Responds to the error and producing an output that is directly proportional to the magnitude of the error.
  - As error approaches zero then Proportional will reach zero
- Integral (I): Cumulative sum of past errors and holds the required magnitude out control signal.
  - Responsible for reducing error

### **Properties**

Proportional Gain  $K_P$ , Integral Gain  $K_i$ 

#### **Proportional Gain**

- Increases responsiveness → higher Kp makes system react faster.
- Reduces steady-state error but cannot eliminate it completely.
- Too high Kp → causes oscillations or even instability.
- Too low Kp → system becomes sluggish.
- Affects rise time (lower rise time with higher Kp).

#### **Integral Gain**

- Eliminates steady-state error completely (good for accuracy).
- Improves tracking performance for constant references.
- Increases overshoot and oscillations if too high.
- Slows down the system response (increases settling time if not tuned properly).

$$V_{dc} = \frac{V_{m}}{2\pi} \left( 1 + \cos \alpha \right)$$

$$d = 0^{\circ} \Rightarrow V_{dc} = \frac{V_{m}}{4\pi} \left( 1 + 1 \right) = \frac{V_{m}}{\pi}$$


$$d = 90^{\circ} \Rightarrow V_{dc} = \frac{V_{m}}{4\pi} \left( 1 + 0 \right) = \frac{V_{m}}{2\pi}$$

$$d = 90^{\circ} \Rightarrow V_{dc} = \frac{V_{m}}{4\pi} \left( 1 + 0 \right) = \frac{V_{m}}{2\pi}$$

$$d = 90^{\circ} \Rightarrow V_{dc} = \frac{V_{m}}{4\pi} \left( 1 + 0 \right) = 0$$

=> As Finning Angle Increases

Output de voltage declar

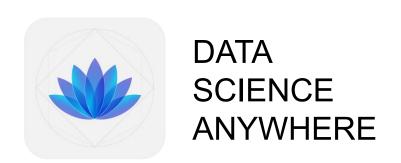





https://www.youtube.com/@datascienceanywhere



https://www.udemy.com/user/freeai-space/



https://github.com/datascienceanywhere



https://vedicskill.com